


# Template Week 3 – Hardware

Student number: 570107


## Bonus point assignment – week 3

Complete the **half adder**, **full adder** and **4-bit adder** assignment as described in the PowerPoint slides of week 3 in Logisim. Save the chip design and also export three PNG pictures of the separate finished designs. See the PowerPoint slides of week 3.

Half adder:

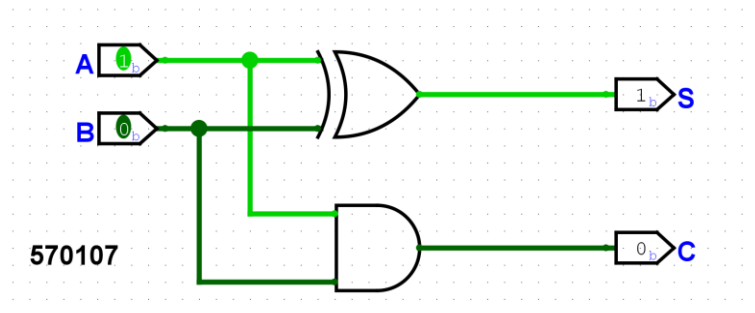

Full adder:

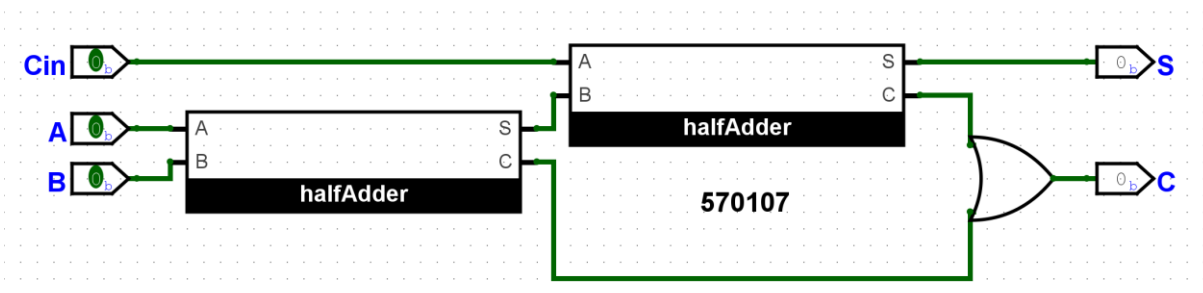

Four bit adder:

